


Circuit Design and Architecture Exploration of FPGAs

1



Topics

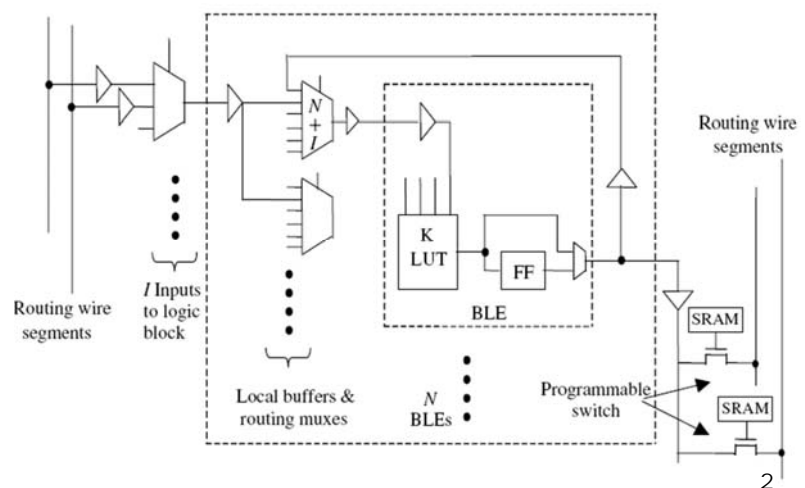
- Circuit Design for FPGAs
- Logic Block Architecture Study
- Routing Architecture Study



2

Lookup Table Circuitry

 
- 2 options for bit-selection
 - decoder or multiplexer?



3

Bit-Selection in Conventional RAM/ROM

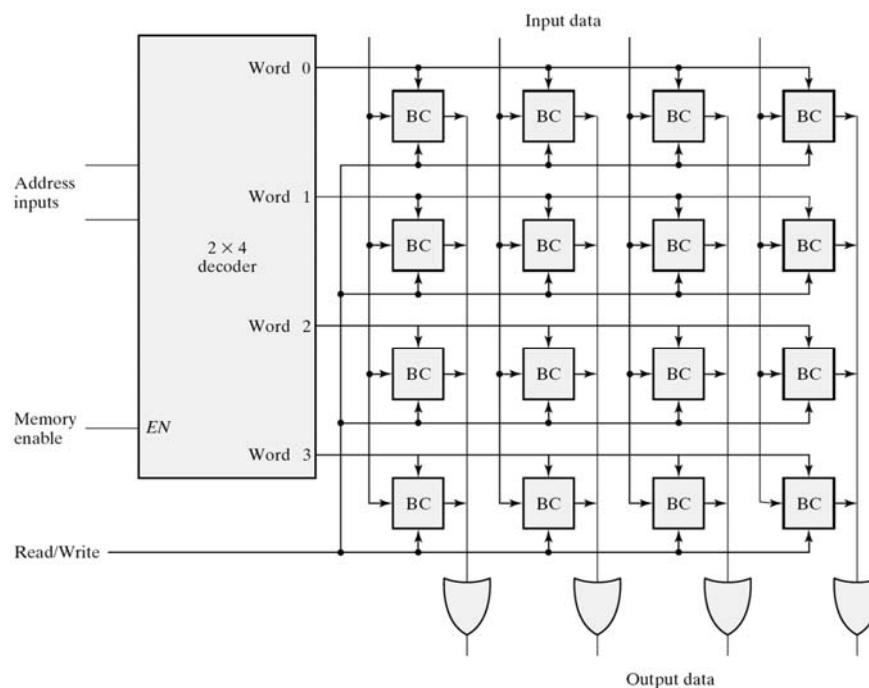
- RAM/ROM typically uses decoder for bit-selection



4

Bit-Selection for LUT

 - FPGA's LUT uses a multiplexer for bit-selection.




- Multiplexer presents smaller load to memory cells.
 - Allows smaller memory cells

5

Multiplexers in FPGA

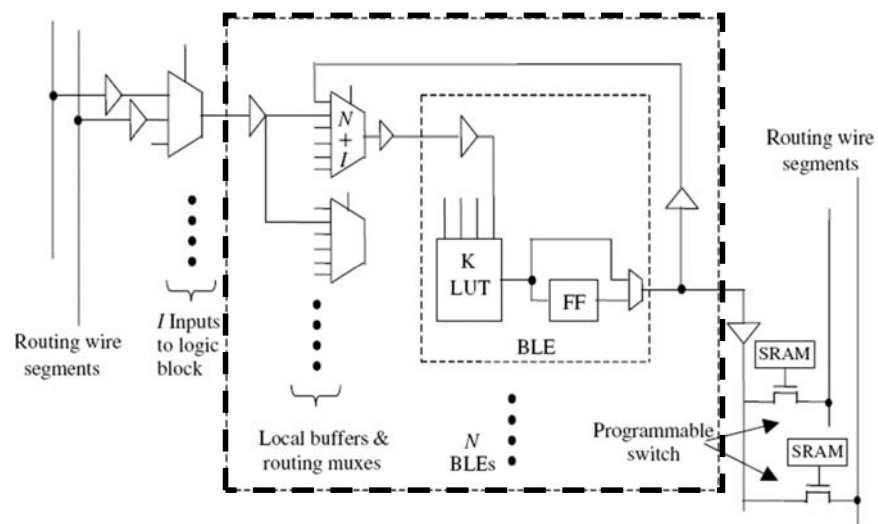
- Muxes used inside LUTs and for routing (intra-block and inter-block).




A logic block and its periphery

6

Multiplexer Design

 

By static gates

 

By pass transistors

7


Multiplexer Design

- Pass transistor multiplexer uses fewer transistors than fully complementary gates.
- Pass transistor is somewhat faster than complementary switch:
 - Equal-strength p-type is 2.5X n-type width.
 - Total resistance is 0.5X, total capacitance is 3.5X.
 - RC delay is $0.5 \times 3.5 = 1.75$ times n-type switch.

8

Performance of Static Gate MUX

 
- Delay through n -input NAND is $(n+2)/3$ using logical effort computation.
- For b -bit mux
 - $\lg b + 1$ inputs at first level, so delay is $(\lg b + 3)/3$.
 - Delay at second level is $(b+2)/3$.
- Delay grows as b .



9

Performance of Tree-based Pass Transistor MUX

 
- Delay proportional to square of path length.
- Delay grows as $(\lg b)^2$.



10

Encoded MUX vs Decoded MUX

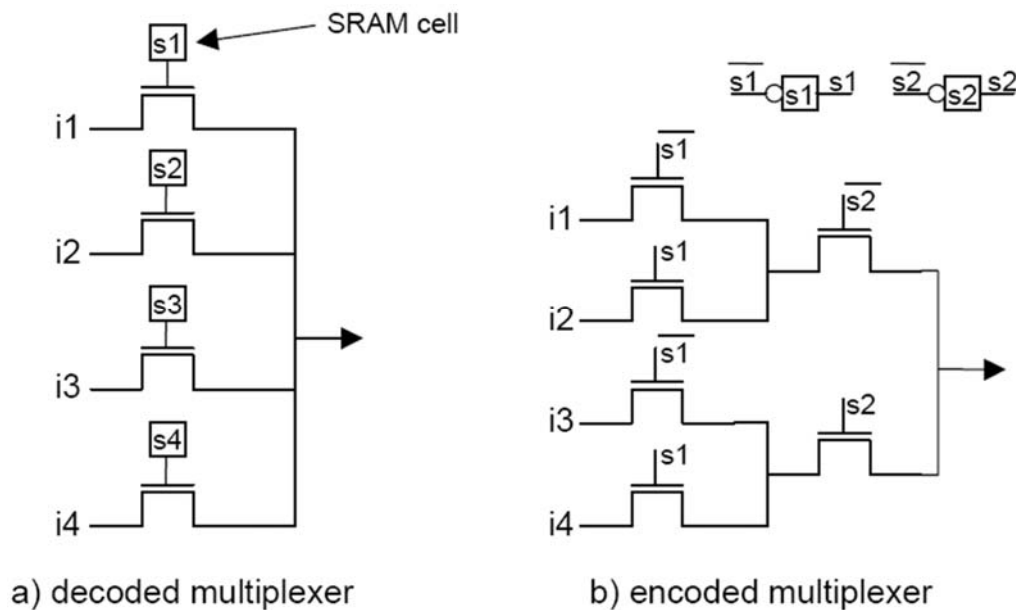
- Tradeoff between transistor count and delay



11


Leakage in MUX-based Routing Switch

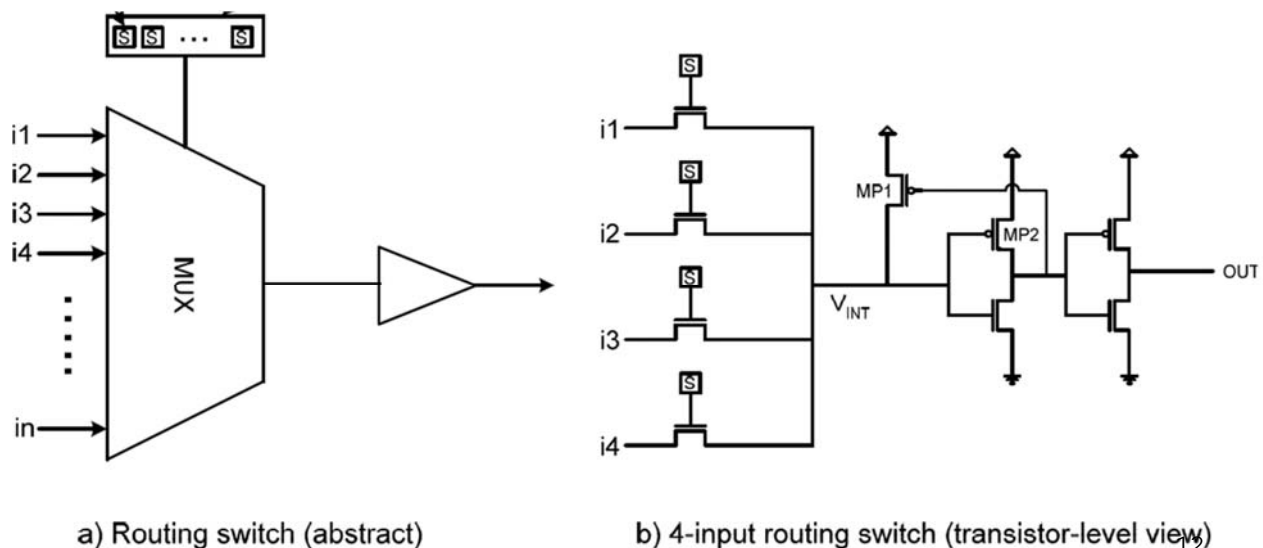- Level restoring buffer to avoid leakage at MP2 due to a weak V_{INT}



MUX-based Routing Switch Design

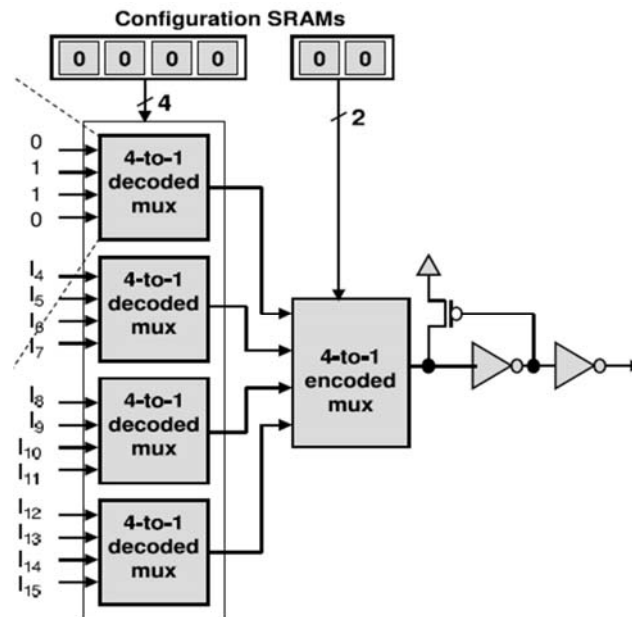- Optimize: transistor count, delay, leakage



13

Architectural Issues


- Granularity of logic elements in the FPGA?
- LE structure:
 - ☐ What functions?
 - ☐ How many inputs?
 - ☐ Dedicated logic?
- What types of interconnect?
 - ☐ How much of each type?
- How long should interconnect segments be?
- How should we vary interconnect?
 - ☐ Uniform or non-uniform over chip?

14

FPGA Architecture Evaluation


Methodology

 - Empirical approach to explore different architectures is typical



15

Logic Block Structure

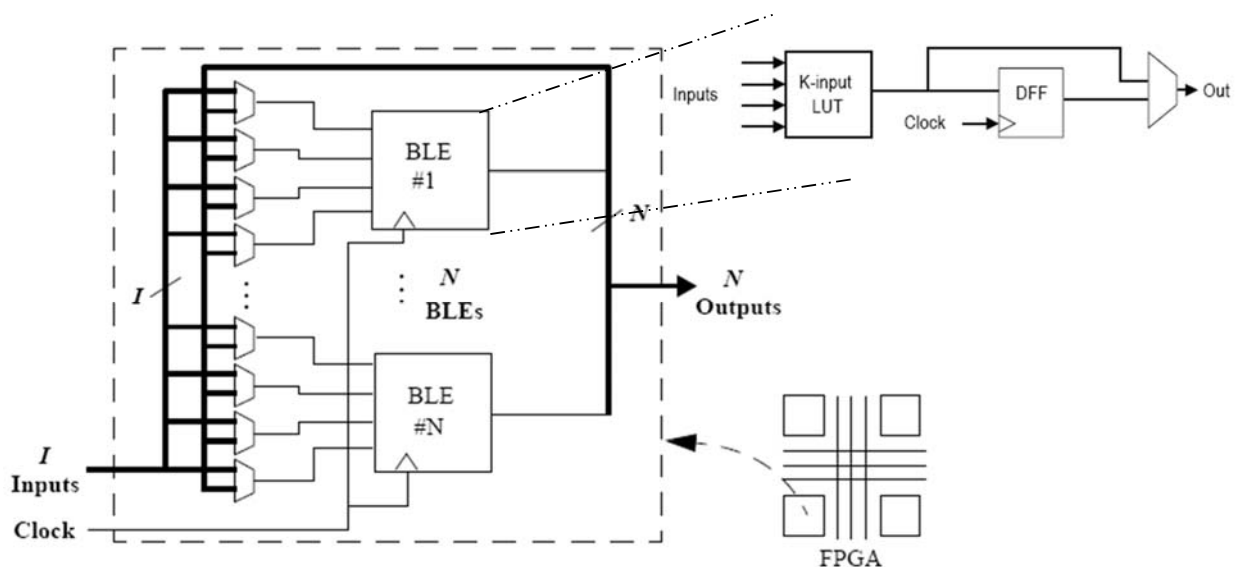

16


Logic Block Granularity Study

- *How large should the LUT size (K) be?*
- Effects on area & speed
 - Area
 - As K increases, fewer logic blocks are needed for a design but area per block increases (LUT's SRAM bits is 2^K)
 - Speed
 - As K increases, each critical path contains fewer blocks but delay per block increases


17

Effect of LUT Size on Area

 - As LUT size (K) increases
 - Total FPGA area first decreases and then increases



 
blocks required & area per block
for different LUT sizes



Total FPGA area for different LUT sizes

Effect of LUT Size on Speed

 - As K increases, each critical path contains fewer blocks but delay per block increases




#LUTs on a critical path & delay per LUT for different LUT sizes

19

Innovative Idea – Adaptive Logic Module

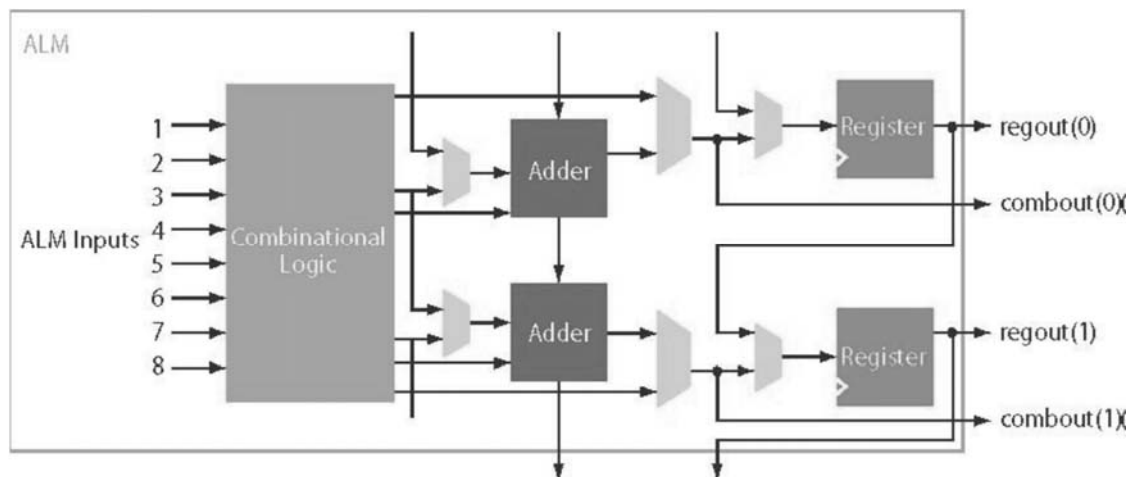
- Altera Stratix ALM (adaptive logic module)



20

Flexibility of Adaptive Logic Module

■ Fracturable into two

 


Output 1	Output 2	Shared inputs (min)
6-LUT	-	-
5-LUT	5-LUT	2
5-LUT	4-LUT	1
5-LUT	3-LUT	0
4-LUT	4-LUT	0
4-LUT	3-LUT	0
3-LUT	3-LUT	0

21

Adaptive Logic Module

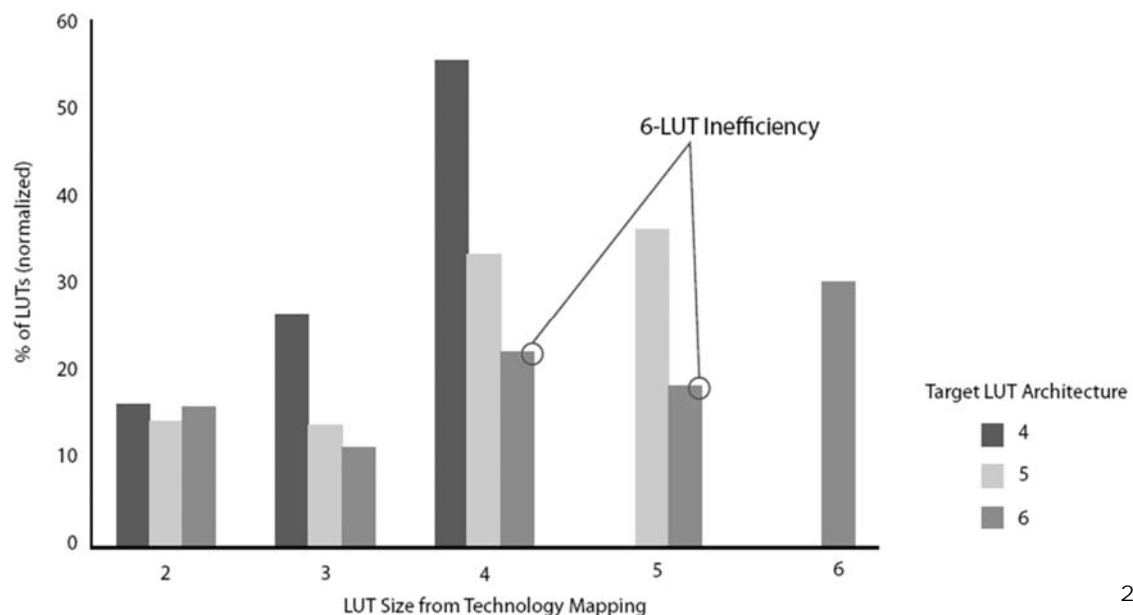
■ *Observation:* Functions generated by synthesis have different input sizes.



22

Advantages of Adaptive Logic Module

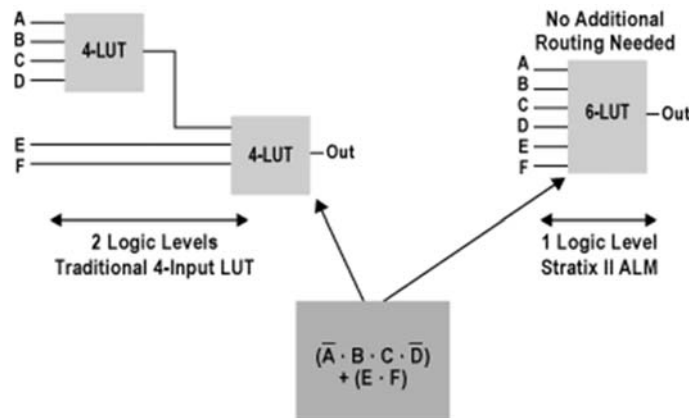
- ALM-based architecture vs traditional 4-LUT-based architecture
 - Improved area efficiency
 - Improved timing performance



23

Logic Block Clustering

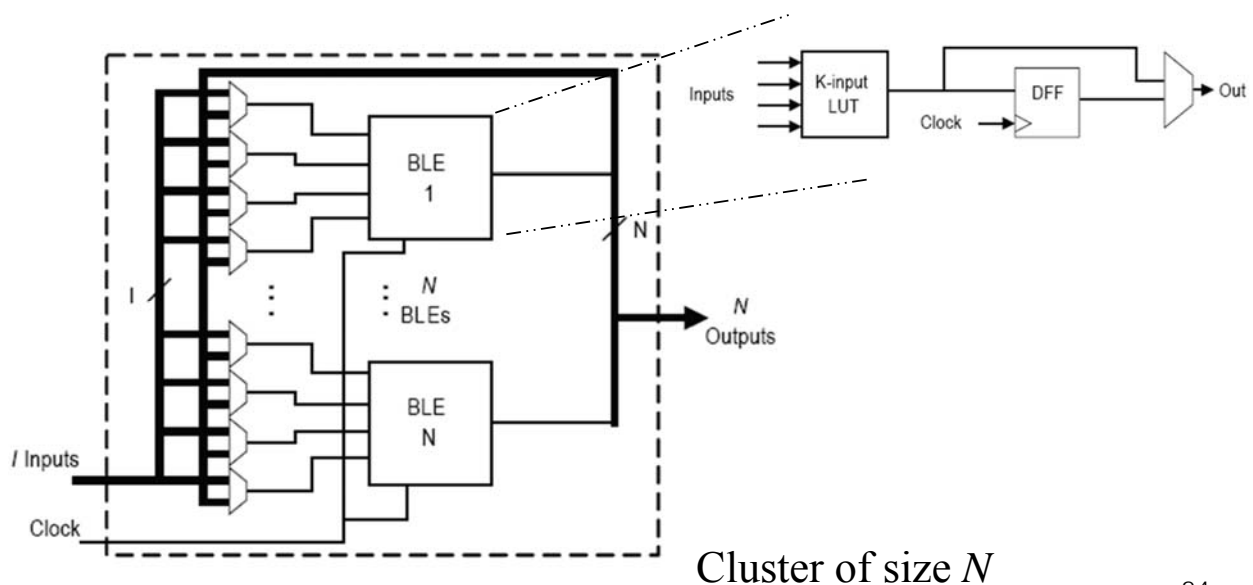
- Logic block made up of a cluster of LUTs and FFs



24


Logic Cluster Study

 - *How many cluster input pins (I) are needed?*
 - BLEs in a cluster often share many input signals
 - Empirically, # input pins I needed to fully utilize a cluster of N K -LUT is
 - $I = K(N+1)/2$



Area Efficiency of Different Cluster Sizes

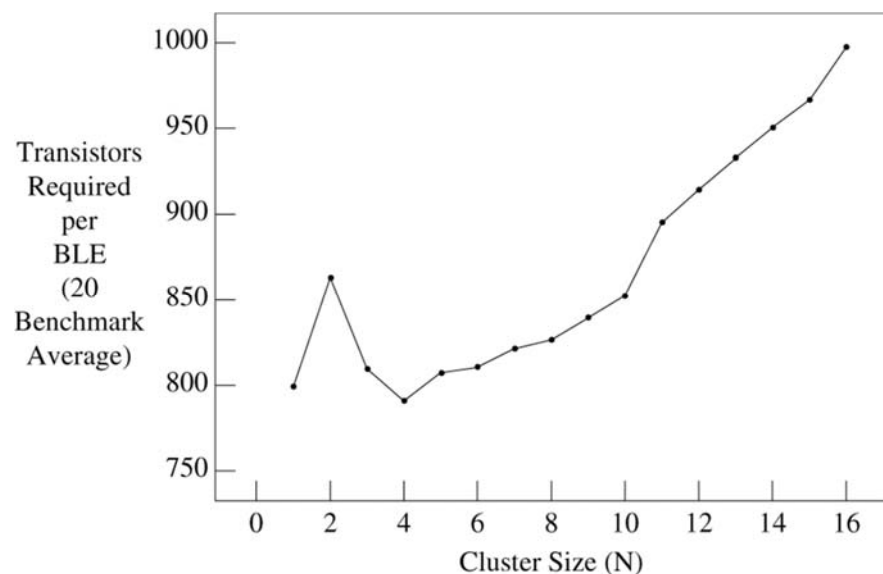
- Clusters in size 1-8 are area-efficient.



Transistors per BLE vs. cluster size (includes overhead circuits)

Effect of Cluster Size and LUT Size on Speed

 - As LUT and cluster size increase, critical path delay monotonically decreases with diminishing returns
- Significant returns to increase LUT size up to 6 and cluster size up to 3 or 4




Critical path delay for different LUT and cluster sizes

27


Programmable Routing

 - Programmable switches connect fixed metal wires



28


Routing Architecture

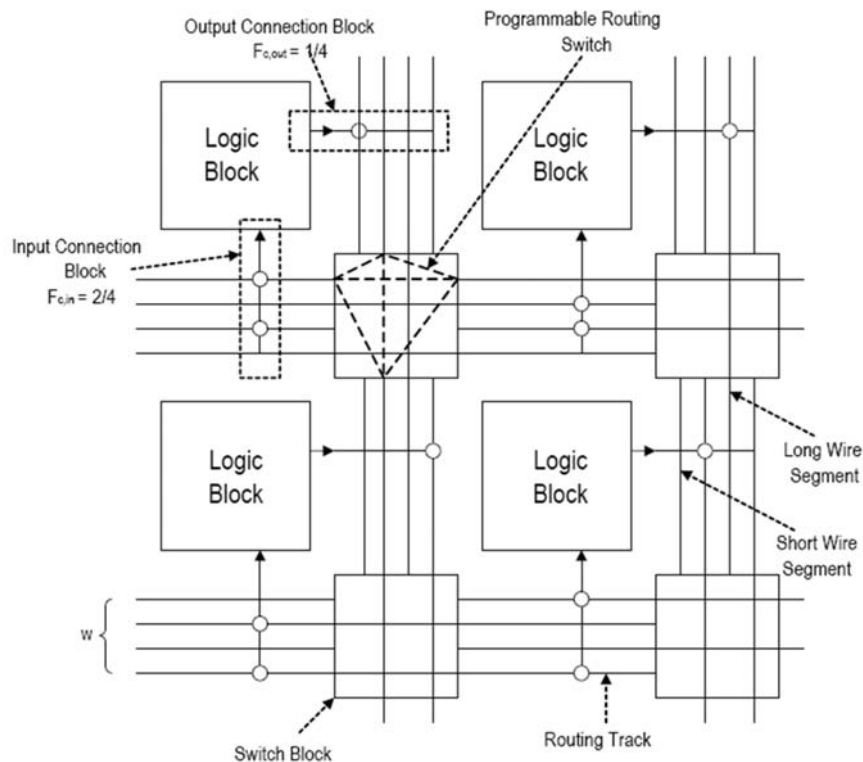

29

Some Parameters of Routing Architecture

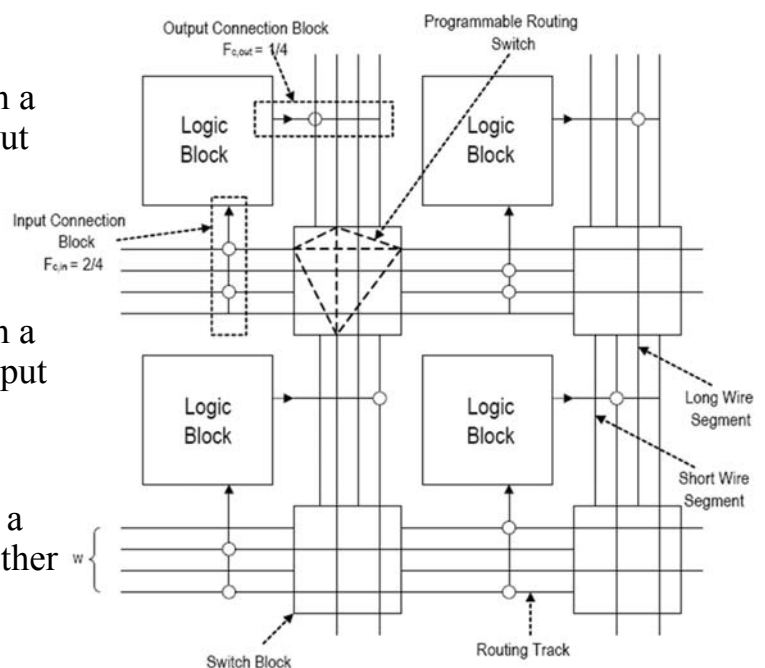
- Input connection block flexibility $F_{c,in}$
 - Fraction of wire segments in a channel connected to an input pin of a block
- Output connection block flexibility $F_{c,out}$
 - Fraction of wire segments in a channel connected to an output pin of a block
- Switch block flexibility F_s
 - No. of possible connections a wire segment can make to other wire segments



30

2 Types of Routing Switches

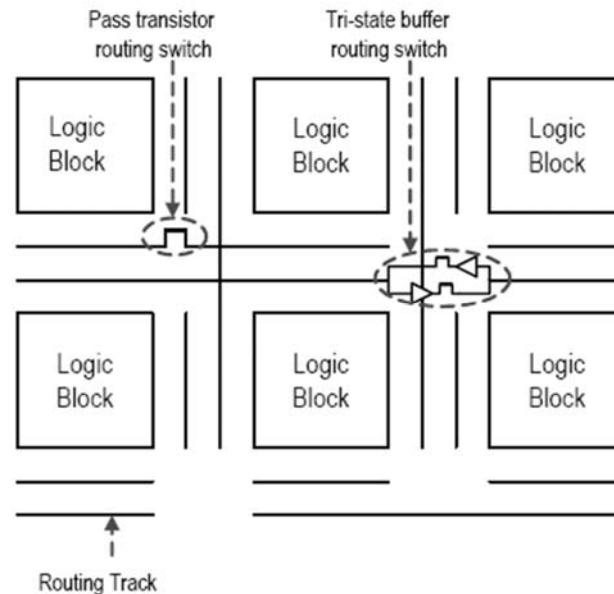
- Typically, mix pass transistor switches & tri-state buffer switches (*why?*)



31

Pass Transistor Routing Switch

 - Small area
- Resistive switch
- Faster for short paths
- Delay grows as the square of no. of switches



32

Tri-state Buffer Routing Switch

- Larger area
- Regenerative driver
- Faster for long paths passing through many switches
- Delay grows linearly as no. of switches



33


Other Routing Architecture Factors and Parameters

- Speed, Area and Power also depend on
 - ☐ Channel segmentation
 - ☐ Transistor size
 - ☐ Buffer size
 - ☐ Ratio of pass transistor switches & tri-state buffer switches
 - ☐ Metal width
 - ☐ Wire spacing
 - ☐ ...

34

Connectivity

 - What is the # hops required to get from one logic block to another?
- Fewer hops → better performance
- More predictable pattern → easier CAD tool optimization




Stratix FPGA series connectivity

35

Clock Nets

- Must drive all LEs.

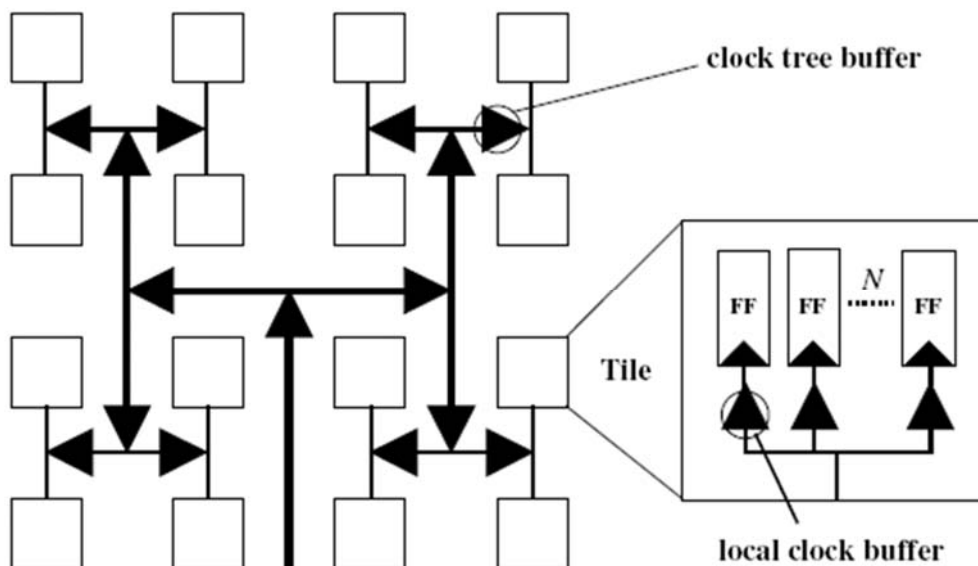

36




-

Track Distribution

Pinout

■ How many pins?

 - ☐ Limited by technology.
- ☐ Too much logic, not enough pins means we can't get signals off-chip.
- ☐ Too many pins means logic won't be fully utilized.



39

Rent's Rule

- Developed by E. F. Rent (IBM) in 1960.
 - ☐ Experimentally derived from sample designs.
- Number of pins vs. number of components is a line on a log-log plot:
 - ☐ $N_p = K_p N_s^\beta$
- Parameters may vary based on technology:
 - ☐ Rent measured $\beta = 0.6$, $K_p = 2.5$.
 - ☐ Modern microprocessor has $\beta = 0.455$, $K_p = 0.82$.

40



FPGAs and Pins

- Chip capacity is growing faster than package pinout.
- Harder to use logic in a multi-FPGA design
 - must try to fit a large function with a small interface into the FPGA
 - may use time-division multiplexing for I/Os

41



References

- “Leakage Control in FPGA Routing Fabric”, in *ASP-DAC’05*.
- “The Effect of LUT and Cluster Size on Deep-Submicron FPGA Performance and Density”, in *FPGA’00*.
- “Improving FPGA Performance and Area Using an Adaptive Logic Module”, in *FPL’04*.
- “Flexibility of interconnection structures for field programmable gate arrays”, *IEEE J. Solid-State Circuits*, vol. 26(3), 1991.
- “Mixing Buffers and Pass Transistors in FPGA Routing Architectures”, in *FPGA’01*.
- “FPGA Architecture: Survey and Challenges”, *Foundations and Trends in Electronic Design Automation*, vol.2(2), 2007.
- “VPR 5.0: FPGA CAD and Architecture Exploration Tools with Single-Driver Routing, Heterogeneity and Process Scaling”, in *FPGA’09*.

42